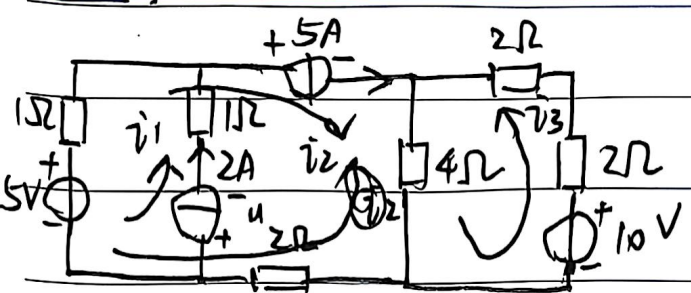


17



$$\left. \begin{aligned} i_1 &= 2A \\ i_2 &= 5A \end{aligned} \right\}$$

$$i_3 = 8A \quad 10V$$

$$i_3 \cdot 8\Omega + i_2 \cdot 4\Omega - 10V = 0$$

$$\Rightarrow i_3 = 1.25A$$

$$P_{5V} = \cancel{7.5W} (i_1 - i_2) \cdot 5V = -15W$$

$$P_{10V} = -i_3 \cdot 10V = 12.5W$$

$$5 + u_{2A} + 2i_1 - i_2 = 0 \Rightarrow u_{2A} = -4V$$


$$\therefore P_{2A} = u_{2A} \cdot i_1 = -8W$$

$$u_{5A} + u_{2A} + i_2 + i_1 + 4i_3 = 0 \Rightarrow u_{5A} = \cancel{23V} -23V$$

$$\therefore P_{5A} = u_{5A} \cdot i_2 = -115W$$

u_a, u_b, u_c, u_i, i

18

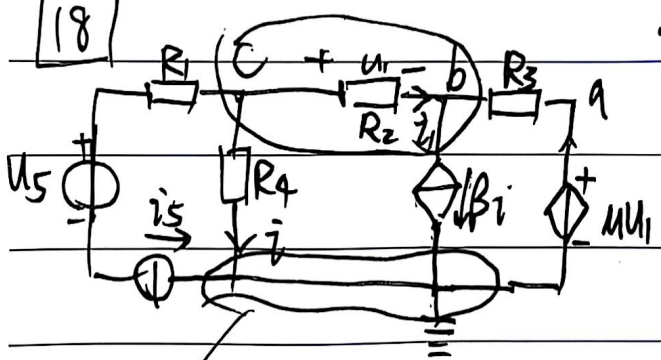

a: $u_a = u_1$

b+c: $\frac{u_b - u_1}{R_3} + \frac{u_c}{R_4} = -\beta i - i_5$

pt: $u_c = i R_4$

$u_c - u_b = u_1$

~~u_c~~

$$u_1 = i_1 R_2$$

$$i_1 = \beta i - \frac{u_1}{R_3}$$

$$\Rightarrow u_1 = \beta i R_2 - \frac{u_1 R_2}{R_3} u_1 \quad D$$

$$KCL: i + i_5 + \beta i - \frac{u_1}{R_3} = 0 \quad (2)$$

$$\Rightarrow u_1 = \frac{R_2 R_3 i_5 \beta}{R_3 \beta - R_3 - u_1 R_2} = \frac{\beta R_2}{1 + \beta} i_5 = \frac{\beta R_2}{1 + \beta} \frac{u}{R_3} - 1 - \frac{u R_2}{R_3}$$